ourdiu.com | Shared by SUPAN ROY

	Digital Logic Design Spring 2025 Quiz 4 Section: 65_E	
1.	Draw the diagram and truth table of a. Controlled D Latch b. JK Flip-Flop c. SR Latch	[4+4+3=11]
2.	Draw the *figure* and *timing diagram* of a 2-bit asynchronous down counter.	[4]

ourdiu.com

*This is not the actual question file. We got the image but not in good condition. So, re-written in this file.