ourdiu.com | Shared by Prahalad Mondal Ullash

Daffodil International University

Faculty of Science & Information Technology

Department of Computer Science and Engineering

Final Examination, Summer - 2026

Course Code: CSE215 Course Title: Electronic Devices and Circuits

Level: 2 Term: 2 Batch: 68

Exam Duration:2 Hours **Marks: 40**

Answer ALL Questions

[The figures in the right margin indicate the full marks and corresponding course outcomes. All portions of each question must be answered sequentially.]

1.	***a)***	**Draw** the block diagram of multistage amplifier.	[2]	CO1
	b)	**Define** feedback and state its significance in electronic amplifiers.	[2]	
	c)	**Define** faithful amplification and state the conditions required to achieve it.	[2]	
	d)	**State the** role of Emitter bypass capacitor (C_E) and Coupling capacitor (C_C).	[2]	
	e)	**List** the Ideal characteristics of OP-Amp.	[2]	
2.	***a)***	**Describe** the working principle of E-MOSFET with necessary diagram.	[5]	CO2
	b)	**Discuss** tank circuit with necessary circuit diagram.	[5]	
3.	***a)***	A 1 pF capacitor is available. Calculate the inductor values in a Hartley oscillator so that f = 1 MHz and m_v = 0.2.	[5]	CO3
	b)	In a transistor circuit shown in Fig. 01, determine the operating point. Assume silicon transistor is used.	[5]	

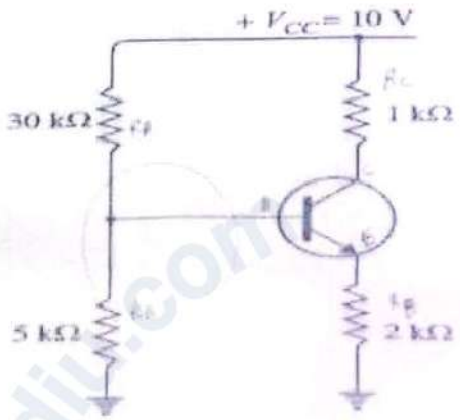


Fig. 01

ourdiu.com | Shared by Prahalad Mondal Ullash

	c)	An amplifier has an open-loop gain Av = 100,000. Negative feedback of 10 db is applied. Solve for: (i) voltage gain with feedback (ii) value of feedback fraction m_v.	[5]	
	d)	Determine the value of I_C for voltage divider method if V_{CC} = 9V, R_E = 1kΩ, R_1 = 39 kΩ, R_2 = 10 kΩ, R_C = 2.7 kΩ, V_{BE} = 0.15 V and β = 90.	[5]	

ourdiu.com