ourdiu.com | Shared by Sadik-ul Imam Khan Ra'ad

Daffodil International University
Department of Electrical and Electronic Engineering
Faculty of Engineering
Final Examination, Fall – 2025

Course Code: 0713-223
Section: A, B, C
Full Marks: 40

Course Title: Energy Conversion II
Level-Term: L2-T2
Exam Date: December 17, 2025

Teacher's Initial: NR
Time: 2 Hours

Notes: Answer all the questions below. The second right most column indicates the course outcomes with respective Bloom's level and the right most column indicates the allocated marks.

Q1.	**Illustrate** the constructional arrangement of different types of DC generators with their circuit diagrams and the voltage and current equations associated with each type.	CO-1 C(2)	5
Q2.	Briefly **describe** the followings with necessary curve for series DC motor, (i) Electrical Characteristic (ii) Mechanical Characteristic	CO-1 C(2)	5
Q3.	**Analyze** how variations in field current affect the operation of a synchronous motor, and **justify** your analysis using an appropriate phasor diagram.	CO-2 C(4)	5
Q4.	**Analyze** the commutation process in a DC generator with necessary illustrative diagrams. Also, **examine** the causes of sparking or fire in commutators.	CO-2 C(4)	5
Q5.	A shunt generator has a full load current of 196 A at 220 V. The stray losses are 720 W and the shunt field coil resistance is 55 Ω. If it has a full load efficiency of 88%, **evaluate** the armature resistance. Also, **evaluate** the load current that corresponds to maximum efficiency.	CO-3 C(3)	5
Q6.	A 4-pole, 250 V d.c. series motor takes 20 A and runs at 900 r.p.m. Each field coil has resistance of 0.025 ohm and the resistance of the armature is 0.1 ohm. **Determine** the speed that run the motor by developing the same torque if: (i) rearranging the field coils in two series and parallel groups Assume unsaturated magnetic operation.	CO-3 C(3)	5
Q7.	A d.c. shunt machine generates 250-V on open circuit at 1000 r.p.m. Effective armature resistance is 0.5 Ω, field resistance is 250 Ω, input to machine running as a motor on no load is 4 A at 250 V. **Calculate** speed of machine as a motor taking 40 A at 250 V. Armature reaction weakens field by 4%.	CO-3 C(3)	5

ourdiu.com | Shared by Sadik-ul Imam Khan Ra'ad

Q8. A 2300-V 1000-hp 0.8-PF leading 60-Hz two-pole Y-connected synchronous motor has a synchronous reactance of 2.8 Ω and an armature resistance of 0.4 Ω. At 60 Hz, its friction and windage losses are 24 kW, and its core losses are 18 kW. The field circuit has a dc voltage of 200 V, and the maximum I_F is 10 A. Answer the following questions about the motor, assuming that it is being supplied by an infinite bus. CO-3 C(5) 5

(i) **Evaluate** I_A and E_A with angle if this machine operates at unity power factor when supplying full load.

(ii) **Determine** the motor's efficiency at full load and unity power factor.

(iii) If the flux were increased by 2.83 %, **calculate** the new armature current.

ourdiu.com