ourdiu.com | Shared by Md Alif Rabbi

Daffodil International University

Department of Computer Science and Engineering


Faculty: FSIT


Quiz Exam 1 , Summer 2026

Course Title: Instrumentation And Control


Time: 30mins Marks: 15

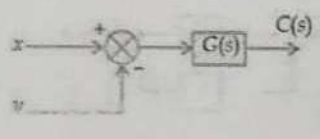a)Define the output of below two figure . Marks 5



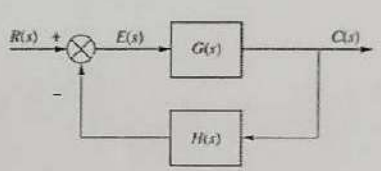

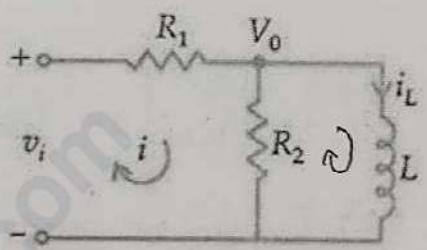b) Draw the block diagram for the below circuit using laplace law. Mark 5



c) Derive the transfer function using block reduction technique.

