ourdiu.com | Shared by Md. Tarekul Islam Limon

Daffodil International University

Faculty of Science & Information Technology

Department of Computer Science & Engineering

Midterm Examination, Fall 2026

LIMON_261

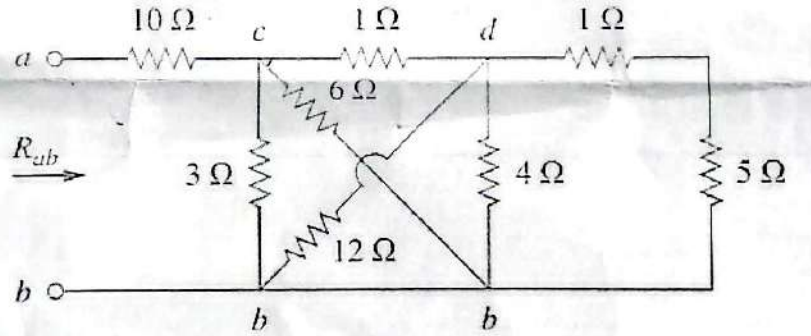
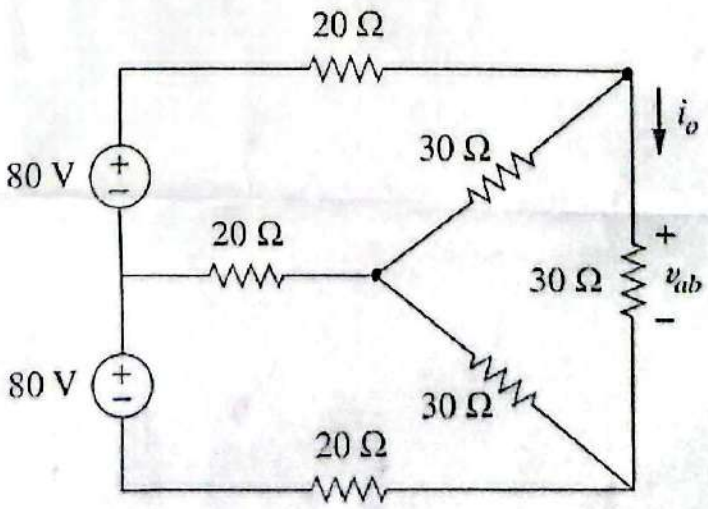
Course Code: CSE121 **Course Title: Electrical Circuits**

Level: 1 **Term: 3** **Batch: 71**

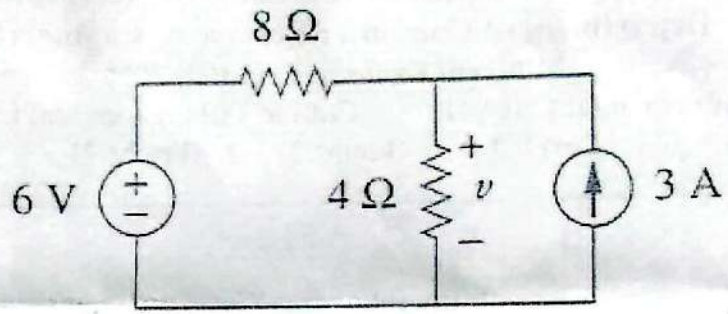
Time: 1:30 Hrs **Full Marks: 25**

Answer all the following *Three* questions

[All portions of each question must be answered sequentially]

Q1.	a.	Define an electrical circuit with a simple diagram.	5x1 =5	CO1
	b.	State DC and AC current and show them in the time domain.		
	c.	Define a dependent current source with a symbol.		
	d.	Define a loop and a mesh in an electrical circuit.		
	e.	Write a short note on Thevenin's Theorem.		
Q2.	a.	Solve for the total current of the following circuit, if a voltage source of 22.4 V is applied between the points a and b : 	2x5 =10	CO2
	b.	Apply mesh analysis to determine the current i_o and the voltage v_{ab} in the following circuit : 		

ourdiu.com | Shared by Md. Tarekul Islam Limon

Q3.	a	Analyze the following circuit using the superposition theorem by determining the contribution of each independent source separately and hence finding the output voltage, v : 	2x5 =10	CO3
	b	Analyze the circuit using Norton's theorem by obtaining the Norton equivalent circuit at terminals a and b in the following circuit : 