
ourdiu.com | Shared by Shaker Abdullah

Quiz–1, Course: Electrical Circuit, Course Code: CSE121


Section: 70_M

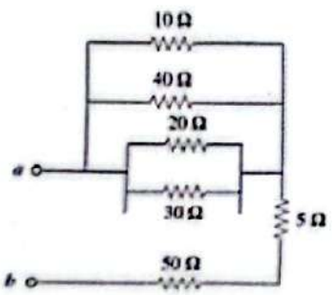1. Find the equivalent resistance at terminals *a-b*



ourdiu.com

ourdiu.com | Shared by Shaker Abdullah

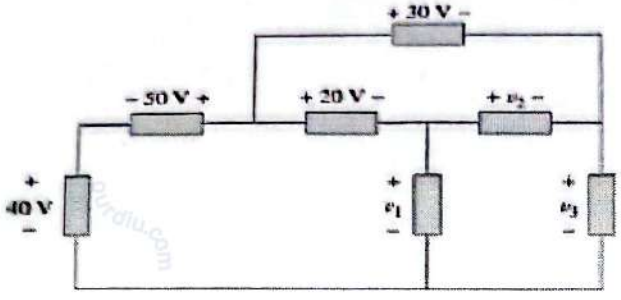2. 

In the circuit obtain v1, v2, v3.