Quiz 2

CSE112: Computer Fundamentals Section: 71_J Marks: 15 Time: 25 min

1. Draw the circuit diagram of the following expression using NAND gate.
   (A'+B)(AB')+BC'
2. Write seven Real-Life Applications of AI.

ourdiu.com

ourdiu.com | Shared by Md. Nahid Hossain