ourdiu.com | Shared by Md. Ashraful Islam

Quiz 1

CSE223: Digital Logic Design Section: 67_A Marks: 15 Time: 25 min

1. Convert the number system $4163.53_7 = ?_5$.
2. Draw circuit diagram using NOR gate
   B+(A'C)+BC'